

## Combinational circuits: ALU

ALU is a combinational circuit  
 outputs depend only on inputs  
 operations performed

AND

OR

ADD

SUB

SLT


Zero (a == b)

This is an ARITHMETIC/logic unit

What about multiplication?

Result depends only on inputs

1	1	1	0	0		
			1	1		Carry
			1	0	1	Multiplicand
						Multiplier
			1	1	1	Partial products
		0	0	0		
	1	1	1			
						Product
1	0	0	0	1	1	

 

(Fig. 4.21)


Can this be done with a combinational circuit?

Sure, but

How big is this truth table?

What would the circuit have to look like?

## Unsigned Combinational Multiplier

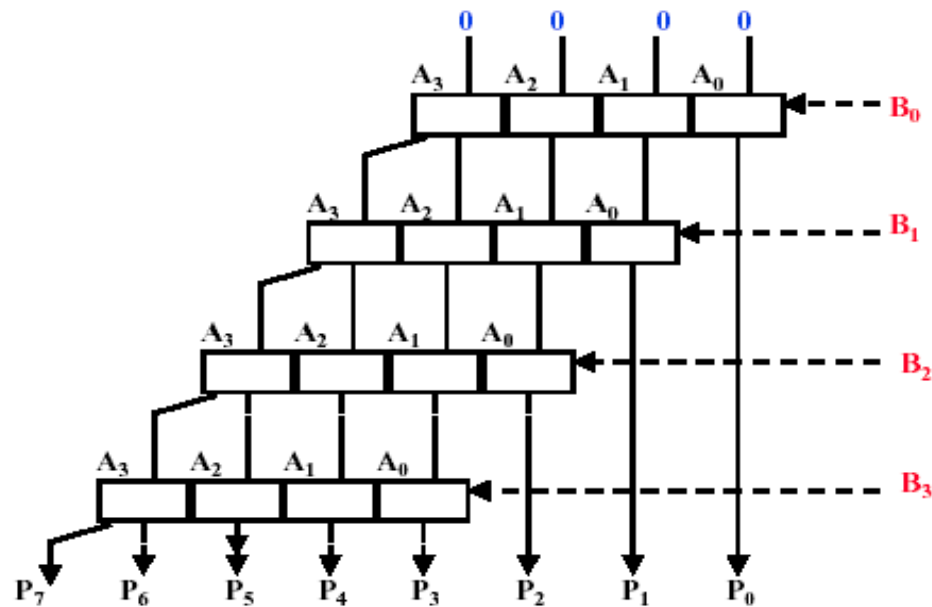

This gets rather large even for 4 bits.

Can we split up the problem in groups of 4?


Reference:

<http://www-inst.eecs.berkeley.edu/~cs152/>
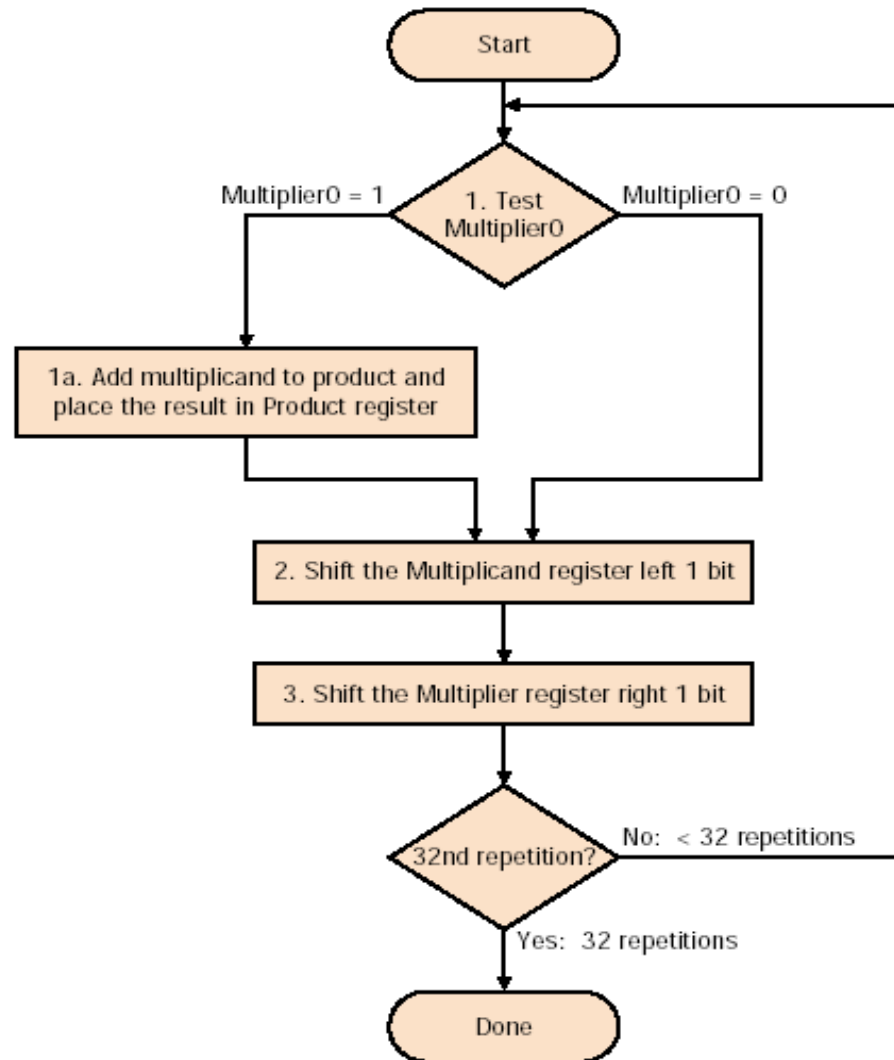
# Multiplier


Better solution: iterate  
(Fig. 4.26)

Add and shift:  
Look at current bit position  
If multiplier bit is 1  
    add multiplicand  
else  
    add 0  
Shift multiplicand



# Multiplier

Multiplier circuit  
(Fig. 4.26)

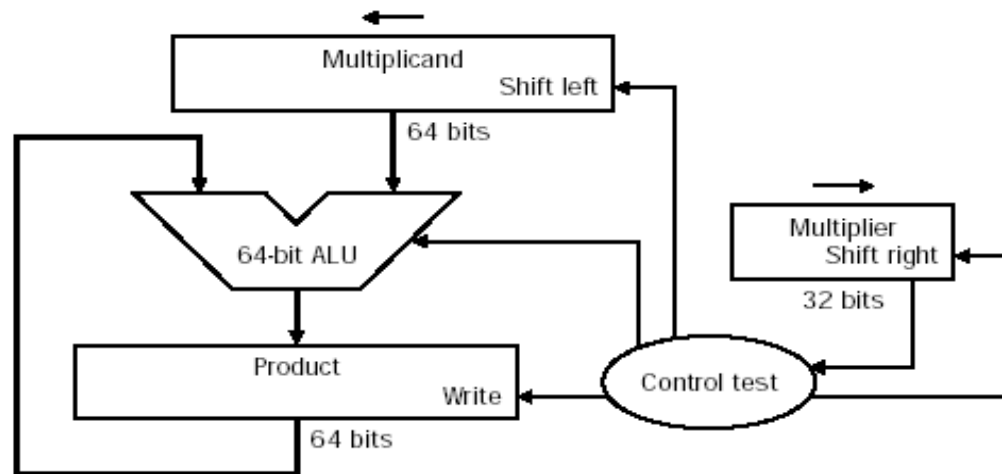

The efficiency of this can be improved, but there is a more fundamental problem:  
How to implement the notions of:  
state (registers)  
update (clock)

## Sequential circuits: state

Mathematical functions have no **state**: inputs combined to produce output, no memory

C/C++ functions may have state: store data from 1 call to another

- static variables

- objects store values in data members

State of a running program

- Values of variables

- Values of registers

- Contents of stack

- Address of current instruction

Hibernate laptop

- Save state of entire machine, including all programs

**Sequential** logic circuits

- Previous history is used together with inputs to produce output

- We don't care HOW previous value was obtained

- State encoded in bits

- Finite number of bits, so finite number of states

## Sequential circuits vs. combinational

### Comparison to combinational

Combinational circuits implement Boolean functions

Input ---> output, no memory

Only data inputs and control inputs determine the output

Example: Coke (um, Pepsi) machine

Assume: price 75 cents, machine only accepts quarters

Action:

deposit quarter ---> no output

deposit quarter ---> no output

deposit quarter ---> drink delivered

Notice that the output was not always the same for the same input

This is not a Boolean function (combinational circuit)

Memory was used to determine output along with input

Example: linked list object

call list.size() method

What is input? empty

Does it always return same value?

No, its output is the current length of the linked list

### Sequential circuit

Inputs: values x, labelled with subscripts

Outputs: values z, labelled with subscripts

**Uses clock, unlike combinational circuit**

**State**

**made up of devices called flip-flops**

**k flip-flops store a k-bit number representing the current state**

**values denoted by q with subscripts**

**Output z computed from**

**inputs x**

**state q**

**Needed:**

**store current state**

**update to new state**

**Circuit elements**

**Combinational logic**

**Clock**

**State storage**

**Example**

<b>state</b>	<b>input</b>	<b>output</b>	<b>new state</b>
00	1	10	11

## Sequential circuits: clock

"Without time, everything would happen at once."

- Anonymous

### Clock

Outside world: way to tell time


Computer: think of a metronome (number of beats, or cycles, per minute)

Measured in MHz or Ghz (millions or billions of cycles per second)

### Timing diagram

x-axis: time

y-axis: voltage

 

values 0 and 1 are represented by low and high voltage

A clock is a device which alternates values between 0 and 1

period: time T

cycle: single alternation between 0 and 1

frequency:  $f = 1/T$ , units of Hz (cycles per second)

1 GHz means  $10^9$  cycles per second

(period is  $10^{-9}$  seconds, which is 1 nanosecond)




## Sequential circuits: clock

### Clock edge

In each cycle, the clock transitions:

0 to 1: positive edge

1 to 0: negative edge

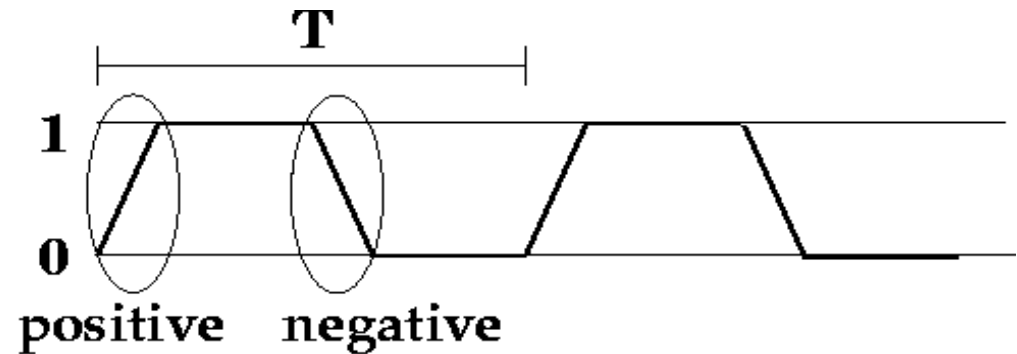

This does not happen instantaneously

rise time: positive edge

fall time: negative edge

Timed devices can only change state on an edge

positive triggered

negative triggered

Otherwise, they hold their value

## Flip-flops

### Basic building blocks

Combinational circuits: gates


Sequential circuits: flip-flops

### Examples of flip-flops

State: flip-flop stores 1 bit

Inputs: control (D or T)  
clock (positive edge)

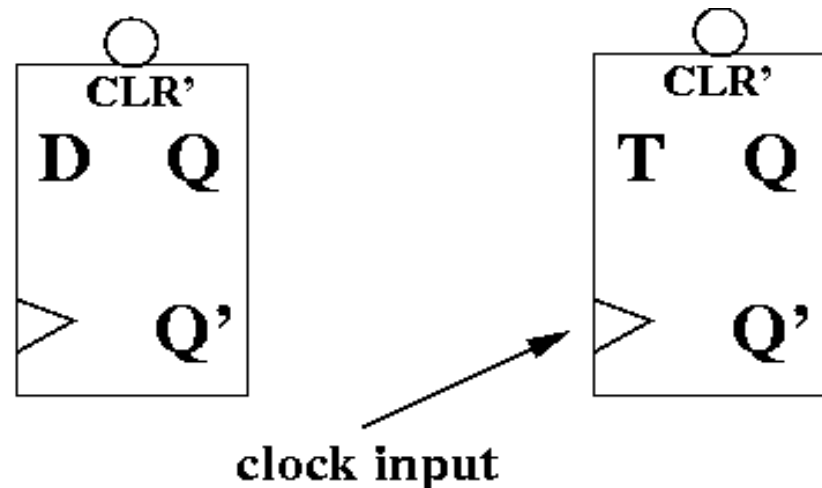Output: Q and Q' (negation)  
Q is current state



### Why both Q and Q'?

Because we can!

Flip-flops can be built with NOR and NAND gates, and the negated output is essentially free

### Additional input (rarely drawn)

CLR': asynchronous clear

When set to 0, Q is immediately (asynchronously) set to 0

This is called active low (consumes less power)

## Flip-flops: latch

How to store a value with a circuit?

Simplest form: unclocked latch

Set-reset (S-R) latch

2 NOR gates with each output fed back

Note that this is not a valid combinational circuit  
(contains a loop)

Assume:

$R = 0$

$S = 0$

$Q = 1$


Then output  $Q$  is fed back as input to the second NOR gate and negated,  
producing the negation  $Q' = 0$

Likewise, the output  $Q'$  is fed back to the first NOR gate and negated,  
producing the output  $Q = 1$

The output can be changed by asserting the value  $R$  or  $S$ :

If  $S = 1$ , then the second NOR gate produces 0, so  $Q$  continues to be 1

 But, if  $R = 1$ , then the first NOR gate produces 0,  
which becomes the new value of  $Q$ .



(Fig. B.12)

## Flip-flops: latch

Characteristic table (corresponds to truth table):

$Q^+$  represents the NEW value of Q


R	S	$Q^+$
0	0	Q
0	1	1
1	0	0
1	1	undefined

When both set and reset are 0, Q is unchanged.

When only S is 1, Q becomes 1.

When only R is 1, Q becomes 0.

 When both R and S are 1, the behavior is undefined.




(Fig. B.12)

## Flip-flops: D (delay)

By adding a clock input C and a control D,  
we can set or reset the latch on a clock signal

Characteristic table for D (delay) flip-flop:

D	Q	Q <sup>+</sup>	Operation
0	0	0	reset
0	1	0	reset
1	0	1	set
1	1	1	set

 

(Fig. B.13)

Note that the second column is actually output, but it is used to generate the next state.  
The third column is the output at a later time.

When the clock value C is 0, then the output of both AND gates is 0, so there is no change.  
(R and S inputs to NOR gates are 0)

When the clock value C is 1, then the output of the AND gates is:  
D' for the first AND gate, and D for the second

This means that D acts as a set when it is 1 and a reset when it is 0.

Notice that this arrangement eliminates the possibility that both set and reset will be 1 at the same time.

## Flip-flops: Toggle (T)

T (toggle) flip-flop holds the value of Q when input T is 0, and toggles when T is 1

Characteristic table for T (toggle) flip-flop:

T	Q	Q <sup>+</sup>	Operation
0	0	0	hold
0	1	1	hold
1	0	1	toggle
1	1	0	toggle

Is this really XOR in disguise?

Inputs of XOR

2 operands

Inputs of T flip-flop

toggle (T)

clock

current state (Q)

Input Q and output Q<sup>+</sup> are really the same output, but at different times

When output changes

Flip-flop can change only at positive clock edge

XOR can change whenever inputs change

## Flip-flops: JK

JK flip-flop has 2 control inputs

Characteristic table for T (toggle) flip-flop:

J	K	Q	Q <sup>+</sup>	Operation	JK	operation
0	0	0	0	hold	0	hold
0	0	1	1	hold	1	reset
0	1	0	0	reset	2	set
0	1	1	0	reset	3	toggle
1	0	0	1	set		
1	0	1	1	set		
1	1	0	1	toggle		
1	1	1	0	toggle		

JK combines functions of D (reset/set) and T (hold/toggle)

This document was created with Win2PDF available at <http://www.daneprairie.com>.  
The unregistered version of Win2PDF is for evaluation or non-commercial use only.