

Finite state machines

Combinational circuit: implements Boolean function

Sequential circuit: implements **finite state machine**

May also contain combinational circuit

In programming languages (i.e., 330), **DFA** (deterministic finite automaton)

Essentially the same, but different purpose

DFA:

Q, a set of **states**

S, a single state which is an element of Q. This is the **start state**.

F, a set of states designated as the **final states**

Sigma, the **input alphabet**

delta, a **transition function** that maps a state and a letter from the input alphabet,
to the next state

DFA is used to recognize a language L, which is composed of a set of strings
made up from an input alphabet

If DFA can recognize strings in the language, then L has a regular grammar

To use DFA:

Start in initial state S

Process each character in the input string, moving from state to state

If DFA in a final state after processing the last character, string in language

Example: alphabet a, b

Is string "aabb" recognized by a DFA?

Finite state machines

Finite state machine (FSM) with output

Q, a set of **states**

S, a single state which is an element of Q. This is the **start state**.

Sigma, the **input alphabet**

Pi, the **output alphabet**

delta, a **transition function** that maps a state and a letter from the input alphabet, to a state and a letter from the output alphabet

Primary differences with FSA:

No final state

Transition function generates output as well as determining next state

Purpose is not to recognize strings, but to generate set of outputs

Describes how inputs and current state generate outputs

For circuits:

Input alphabet: set of k-bit strings

Output alphabet: set of m-bit strings

Transitions from a given state must be:


Mutually exclusive: only 1 choice for any single input value

Exhaustive: all possible inputs have a transition

"Nothing happens": remain in same state

Finite state machines

Example:

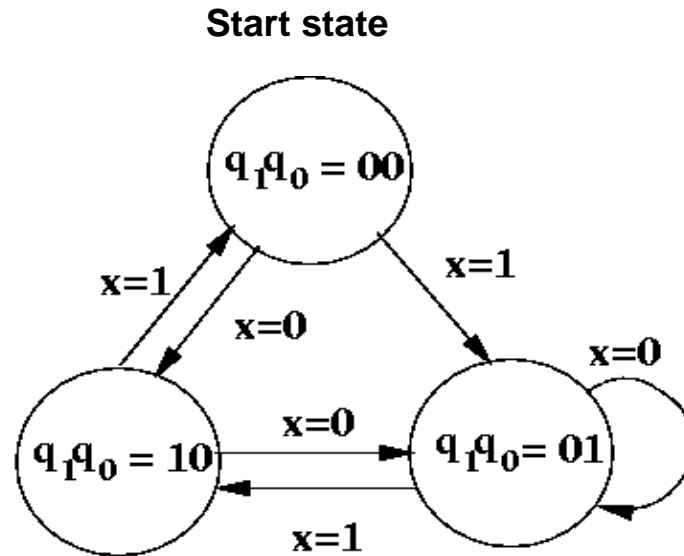

States: represented by circles, 2-bit values q_1q_0

N states require $\text{ceil}(\lg N)$ bits to represent (the ceiling of log base 2 of N)

Inputs: represented by arrows labeled x (number of bits depends on number of transitions)

2^k arrows for k bits of input

Trace:	State	00 (Start)	01	10	01	01	10
	Input	1	1	0	0	1	

Finite state machines: Moore

So far: inputs tell which state to go to next, but no outputs

Moore machines: have outputs for each state


Output for a state is written following the state itself:

01/1 state 01, output 1 $q_1q_0 = 01, z = 1$

number of output bits depends on application

(may be more or less than for state representation)

Example:

 

Input	x		1	1	0	1	1	0
State	q_1	0	0	1	0	1	0	1
	q_0	0	1	0	1	0	0	0
Output	z_1	0	1	1	1	1	0	1
	z_0	1	1	1	1	1	1	1


Finite state machines: Mealy

Moore machines: output is function of state

Mealy machines: output is function of state and input

output is shown on edge

Example:

 

In state 00, input of 1 produces output of 1: 1/1 $x = 1, z = 1$

Notice numbering of states: can select any combination of 2 bits

Input	x		1	1	0	1	1	0
State	q1	0	0	0	1	0	0	1
	q0	0	1	1	1	0	1	1
Output	z	0	1	0	1	1	1	1

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.