
 


## Finite state machines: implementing

Want to implement FSM in circuit:

 

Steps to do this:

1. Create a state transition table
2. Decide how many flip flops you need, and what kind
3. Use the flip flop excitation table to fill out the rest of the chart
4. Implement the circuit

Steps are easy

Hard part: understanding what is going on


## Finite state machines: implementing

State: 2 bits ( $q_1q_0$ )

2 flip-flops to store

Input: 1 bit ( $x$ )

Output: 2 bits ( $z_1z_0$ )

 

### Step 1: State transition table

Start with state and input

Each row represents a state and a possible input value


States before inputs:

Look at every possible input for each state

$q_1$	$q_0$	$x$
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

## Finite state machines: implementing

$q_1$	$q_0$	$x$	$q_1^+$	$q_0^+$
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	d	d
1	1	1	d	d

 

### Step 1: State transition table


#### (a) Write next state

There is no state 11

Put d for "don't care" as next state

## Finite state machines: implementing

$q_1$	$q_0$	$x$	$q_1^+$	$q_0^+$	$z_1$	$z_0$
0	0	0	1	0	0	1
0	0	1	0	1	0	1
0	1	0	0	1	1	1
0	1	1	1	0	1	1
1	0	0	0	1	1	1
1	0	1	0	0	1	1
1	1	0	d	d	d	d
1	1	1	d	d	d	d

 

**Step 1: State transition table**

**(b) Write outputs**

These are just a function of the state

State 11 doesn't exist: "don't care"

## Finite state machines: implementing

Step 2: Pick flip-flops

What kind?

Some combination of D and/or T


Use  $D_1$  to store  $q_1$  and  $T_0$  to store  $q_0$

Step 3: Use the flip-flop excitation tables

to determine D and T

What input for D generates  
an output of 1?

 The entire column for D is a copy of  $q_1^+$



$q_1$	$q_0$	$x$	$q_1^+$	$q_0^+$	$z_1$	$z_0$	$D_1$	$T_0$
0	0	0	1	0	0	1	1	
0	0	1	0	1	0	1	0	
0	1	0	0	1	1	1	0	
0	1	1	1	0	1	1	1	
1	0	0	0	1	1	1	0	
1	0	1	0	0	1	1	0	
1	1	0	d	d	d	d	d	
1	1	1	d	d	d	d	d	


## Finite state machines: implementing

Step 3: Use the flip-flop excitation tables to determine D and T

What value for T do we need to get state 0 from state 0?

What value for T do we need to get state 1 from state 0?

 Fill in rest of column with hold ( $q_0^+ = q_0$ ) or toggle ( $q_0^+ \neq q_0$ )



$q_1$	$q_0$	$x$	$q_1^+$	$q_0^+$	$z_1$	$z_0$	$D_1$	$T_0$
0	0	0	1	0	0	1	1	0
0	0	1	0	1	0	1	0	1
0	1	0	0	1	1	1	0	0
0	1	1	1	0	1	1	1	1
1	0	0	0	1	1	1	0	1
1	0	1	0	0	1	1	0	0
1	1	0	d	d	d	d	d	d
1	1	1	d	d	d	d	d	d

## Finite state machines: implementing

**Step 4: Implement a circuit to generate the control signals**

**One way to do this: use a ROM (read-only memory)**

**Input to ROM: k-bit address**

**Output from ROM: contents of location at given address**

**Number of bits needed for address: inputs to truth table**

**2 bits for state + 1 bit for input in this case**


**Number of bits at each location: number of output bits + number of flip-flops**

**4 bits in this case**

$q_1$	$q_0$	$x$	$q_1^+$	$q_0^+$	$z_1$	$z_0$	$D_1$	$T_0$
0	0	0	1	0	0	1	1	0
0	0	1	0	1	0	1	0	1
0	1	0	0	1	1	1	0	0
0	1	1	1	0	1	1	1	1
1	0	0	0	1	1	1	0	1
1	0	1	0	0	1	1	0	0
1	1	0	d	d	d	d	d	d
1	1	1	d	d	d	d	d	d
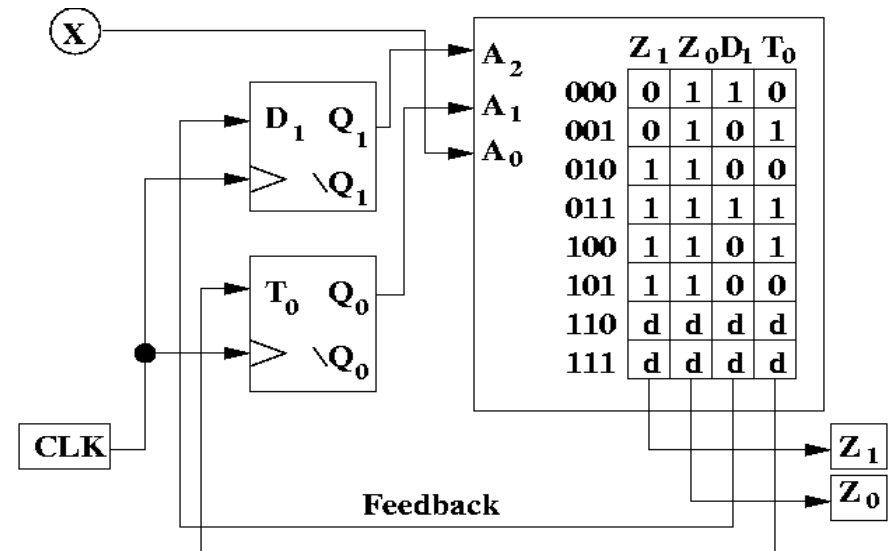
## Finite state machines: implementing


Step 4: Implement a circuit to generate  
the control signals  
Copy last 4 columns to ROM  
Connect inputs and outputs



q <sub>1</sub>	q <sub>0</sub>	x	q <sub>1</sub> <sup>+</sup>	q <sub>0</sub> <sup>+</sup>	z <sub>1</sub>	z <sub>0</sub>	D <sub>1</sub>	T <sub>0</sub>
0	0	0	1	0	0	1	1	0
0	0	1	0	1	0	1	0	1
0	1	0	0	1	1	1	0	0
0	1	1	1	0	1	1	1	1
1	0	0	0	1	1	1	0	1
1	0	1	0	0	1	1	0	0
1	1	0	d	d	d	d	d	d
1	1	1	d	d	d	d	d	d



## Finite state machines: implementing

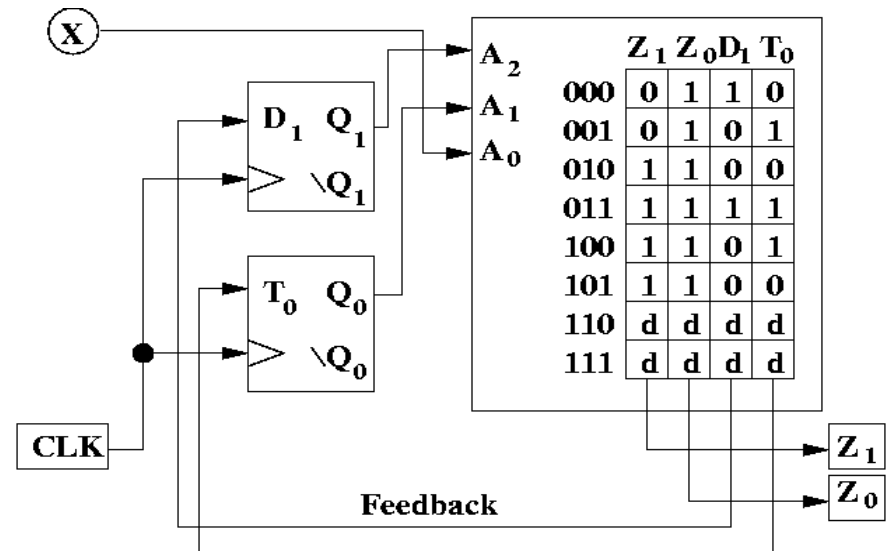

Notes:

Label the address bits:  $A_2A_1A_0$

Connect inputs to address bits in order:  $q_1q_0x$

Label ROM addresses: 000 to 111

Label ROM data columns:  $Z_1Z_0D_1T_0$

Don't include next state in ROM. Where does it go?

$D_1$  and  $T_0$  feed back to flip-flop inputs


Leave the "don't cares" as they are

Circle input  $x$  to show it comes from an external source

Square the outputs  $z$  to show they are external

"Don't forget the stinkin' clock"

## Finite state machines: implementing

 

How it works:

Assume state 00, input 0

Select ROM address 000, data 0110

Output is 01


Next state is determined by  $D_1 = 1, T_0 = 0$

$Q_1$  becomes 1 (D input)

$Q_0$  becomes 0 (hold)

Next state is 10

Try other states and inputs

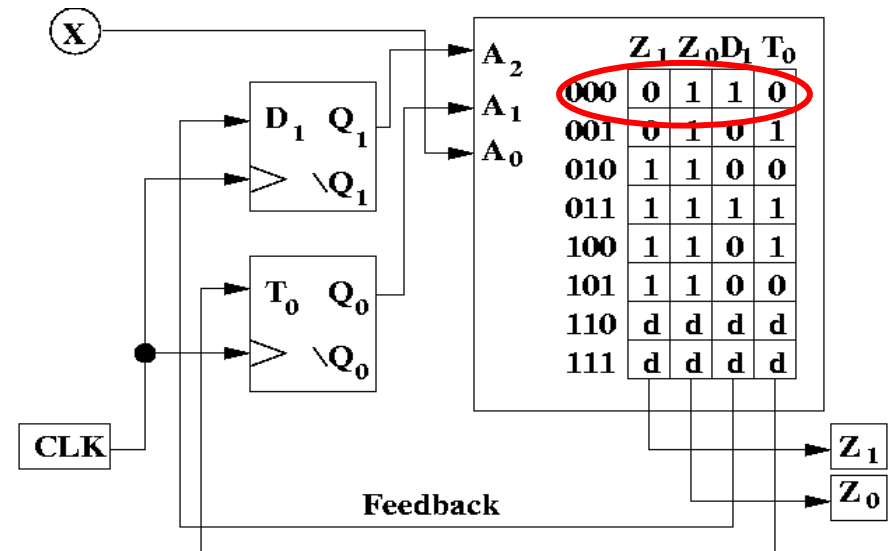

## Finite state machines: implementing

How else could we implement the circuit?

Inputs			Next		Outputs				Minterms
$q_1$	$q_0$	$x$	$q_1^+$	$q_0^+$	$z_1$	$z_0$	$D_1$	$T_0$	$z_1$
0	0	0	1	0	0	1	1	0	
0	0	1	0	1	0	1	0	1	
0	1	0	0	1	1	1	0	0	$\neg q_1 q_0 \neg x$
0	1	1	1	0	1	1	1	1	$\neg q_1 q_0 x$
1	0	0	0	1	1	1	0	1	$q_1 \neg q_0 \neg x$
1	0	1	0	0	1	1	0	0	$q_1 \neg q_0 x$
1	1	0	d	d	d	d	d	d	
1	1	1	d	d	d	d	d	d	

$$z_1 = \neg q_1 q_0 \neg x + \neg q_1 q_0 x + q_1 \neg q_0 \neg x + q_1 \neg q_0 x$$

etc.

Simplified:

$$z_1 = q_1 + q_0$$

$$z_0 = 1$$


$$D_1 = \neg q_1 (\neg q_0 \neg x + q_0 x)$$

$$T_0 = \neg q_1 x + q_1 \neg x$$

Implement using AND and OR gates or PLA

## Finite state machines: implementing

$q_1$	$q_0$	$x$	$q_1^+$	$q_0^+$	$z$
0	0	0	1	1	1
0	0	1	0	1	1
0	1	0	1	1	1
0	1	1	0	1	0
1	0	0	d	d	d
1	0	1	d	d	d
1	1	0	0	1	0
1	1	1	0	0	1

 

In state 01, input of 0 gives state 11 and output 1  
In state 01, input of 1 gives state 01 and output 0  
In state 11, input of 0 gives state 01 and output 0  
In state 11, input of 1 gives state 00 and output 1

Rest of steps:

- pick flip-flops
- use excitation tables
- draw circuit (ROM, gates, or PLA)

This document was created with Win2PDF available at <http://www.daneprairie.com>.  
The unregistered version of Win2PDF is for evaluation or non-commercial use only.