

Single-cycle datapath

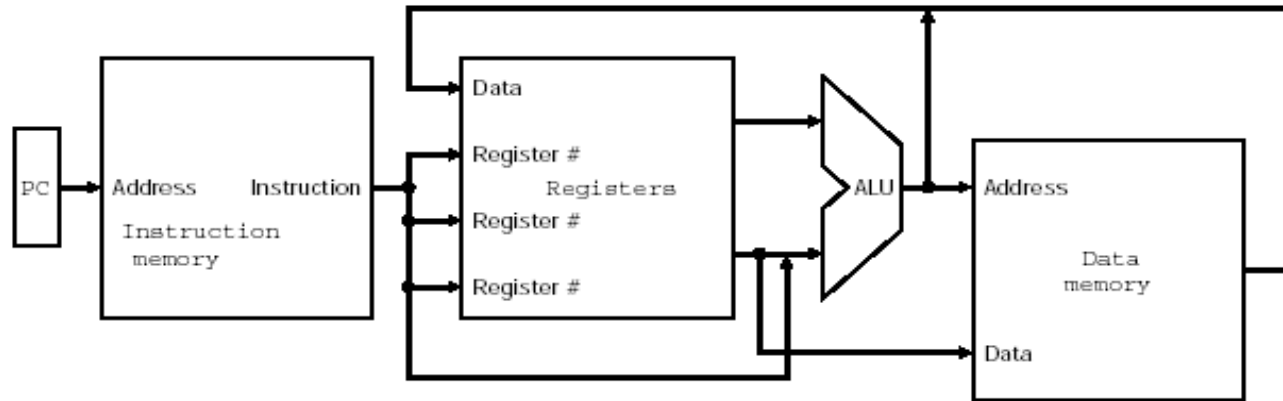


Fig. 5.1

Single-cycle implementation

Assume each instruction is executed in 1 clock cycle

Each component (memory, ALU, etc.) can be used only once

Reason for assuming separate instruction and data memories

Advantage: simpler to design

Disadvantage: speed of machine is determined by time for longest path

Memory access is much slower than register access,
but most instructions use only registers

Better: each instruction type can take different number of clock cycles

Common elements for all instructions

Instruction fetch, PC update

Access 1 or 2 registers

Instruction fetch

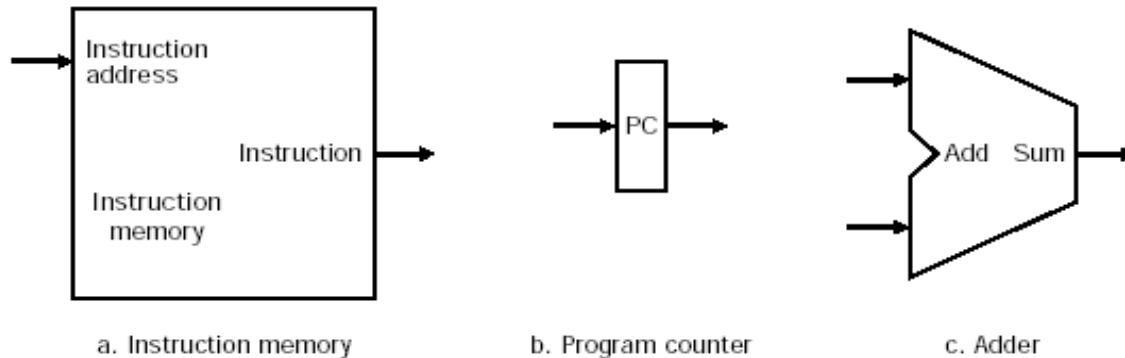


Fig. 5.4

Instruction fetch: used by all instructions

Memory

Input: instruction address

Output: instruction

how to build: defer until later

Program counter

Register containing address of current instruction ("hidden")

Adder: ALU with only one operation

Combinational circuit

Input: 2 operands

Output: sum

Instruction fetch

 


Fig. 5.5

Instruction fetch

PC gives address to instruction memory

Memory outputs instruction contents

Increment PC


PC value is first operand input to adder

Constant 4 is second operand input to adder

PC + 4 is stored back in PC

Repeat once each clock cycle

Register access: R-type

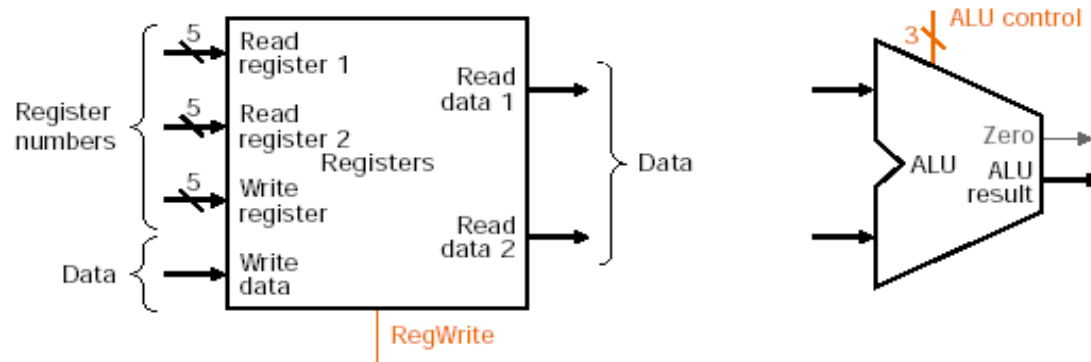

Components

Register file: 32 registers

Inputs

2 read register numbers (5 bits each)

1 write register number (5 bits)

write data (32 bits)

Outputs: 2 read data values (32 bits each)

Control: RegWrite determines whether to write data to target register (1 bit)

ALU: performs arithmetic/logical operations

Inputs: 2 data values (32 bits each)

Outputs


Result of operation (32 bits)

Zero: result is equal to 0 (1 bit)

Control: ALU control selects operation (3 bits)

Fig. 5.6

Register access: R-type

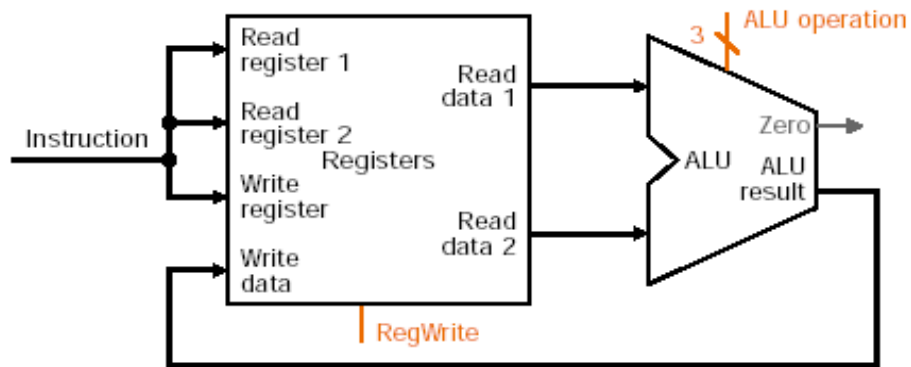

Components

Register file: 32 registers

ALU: performs arithmetic/logical operations

Fig. 5.7

Register read

Instruction gives addresses of 2 read registers and 1 write register to register file
2 data read values are given by register file to inputs of ALU

R-type operation

3 ALU operation control bits are used to determine what operation is required
ALU result is returned to write data input of register file
ALU also has an output called Zero (indicates whether result of operation equals 0)
Note that RegWrite control input is used to determine if result is written to the write register


Single-cycle datapath

The story so far:

Implementing R-type, memory access, and branch/jump instructions


Single-cycle datapath: each instruction takes 1 clock cycle

Common elements:

 

Instruction fetch and PC update

Register access

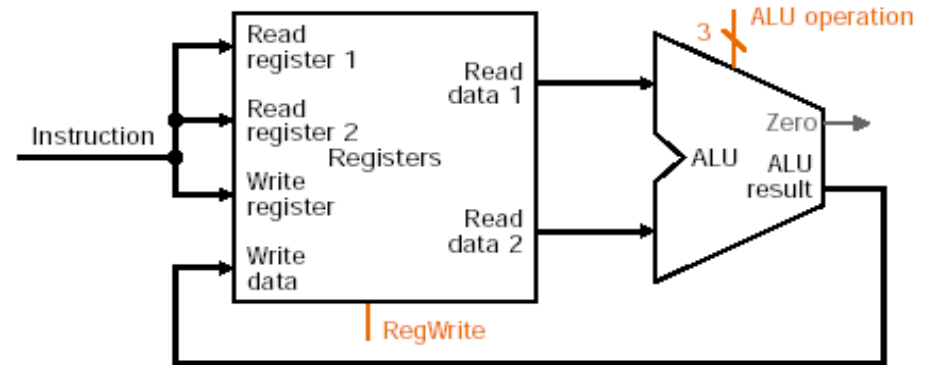

R-type operation: ALU

Load and store

Load and store instructions

```
lw  $rt, offset($rs)
```

```
sw  $rt, offset($rs)
```

Requirements

Add 16-bit offset value to contents of base register \$rs

extend 16-bit value to 32 bits for addition

For load instruction, write value from memory into register \$rt

For store instruction, read data value from register \$rt

Load and store

 


Fig. 5.8

Components

Data memory

Inputs

Address (32 bits)

Write data (32 bits)

Output: Read data (32 bits)

Controls

MemRead

MemWrite

Sign extend

Input: 16 bit data

Output: 32 bit data with sign bit repeated 16 times

Load and store

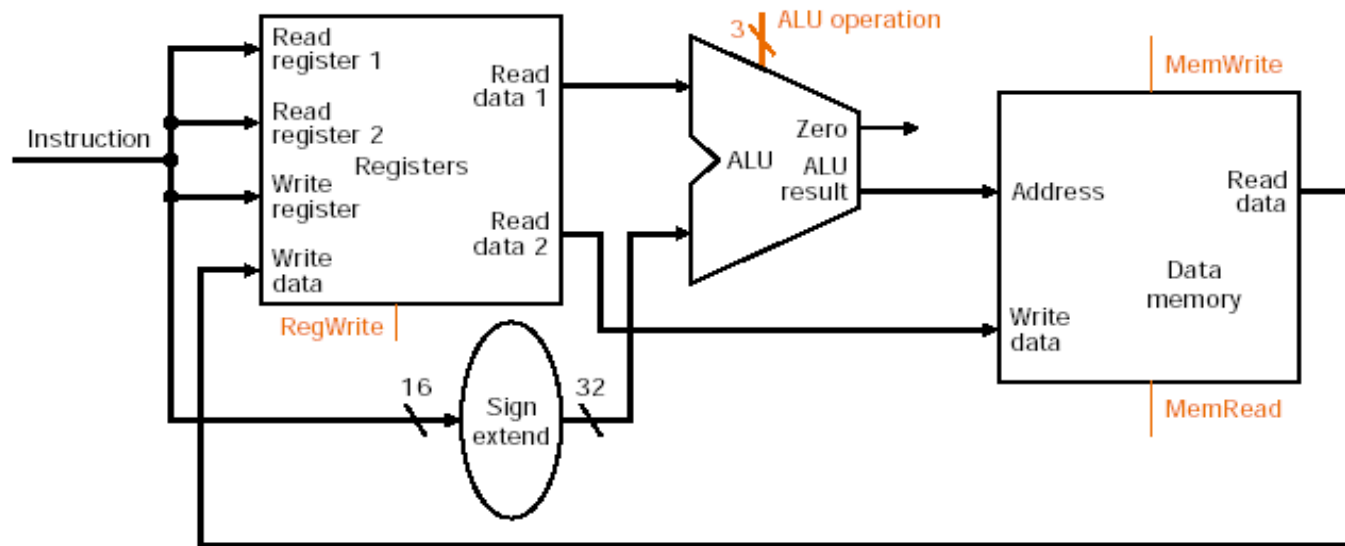


Fig. 5.9

Instruction provides read and write register numbers, 16-bit offset

Register file provides

Read data 1: base register value to ALU

Read data 2: data value to be stored in data memory

Sign extend provides 32-bit offset value to ALU for addition

ALU generates sum of base and offset as address input to data memory

MemRead, MemWrite controls determine whether to read or write data memory

For load (read), data memory provides data for register write

For store (write), data memory writes data to memory location given by address

Branch

Branch on equal

```
beq $rs, $rt, offset
```

Requirements

Compare contents of 2 registers

Shift 16-bit offset left by 2 bits to get word address

Add shifted offset value to value of PC + 4 to get branch target address

Update PC with branch target if operands are equal (branch is taken)

Two operations: compare and add

Also modify instruction fetch datapath to allow PC to be updated with new value

Jump requires different address calculation

Replace lower 28 bits of PC with 26 bits from instruction, shifted left 2 bits

To be added later

Branch

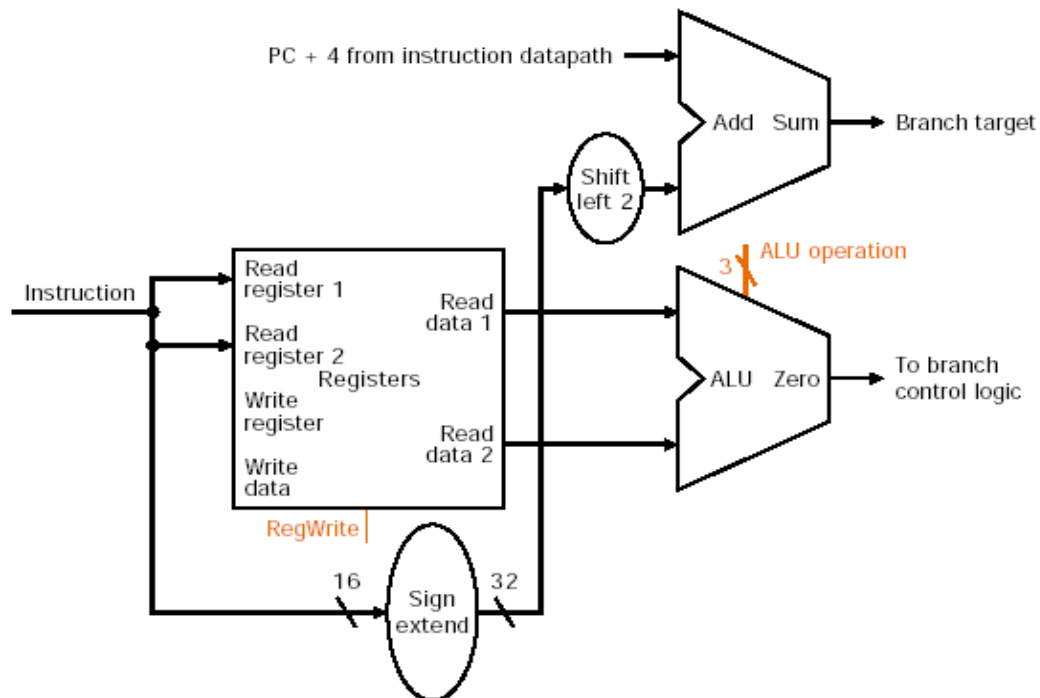


Fig. 5.10

- Instruction provides read register numbers to register file, offset to sign extend
- Registers give operand input to ALU for comparison (which ALU operation?)
- ALU generates Zero output (what value?) to branch control
- Sign extend provides 32-bit value to shifter, which shifts left by 2 bits
- Adder computes branch target for possible PC update using:
 - Offset from shifter
 - PC + 4 from instruction datapath

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.