

Complete implementation

MIPS-lite

arithmetic/logical: `add, sub, and, or, slt`

memory access: `lw, sw`

branch/jump: `beq, j`

Combine datapaths for

instruction fetch (Fig. 5.5)

R-type operations (Fig. 5.7)

Load and store (Fig. 5.9)

Branch (Fig. 5.10)

Jump (to be added)

Add control signals

Version 1: execute each instruction in 1 clock cycle

Version 2: execute each instruction in multiple (shorter) clock cycles

Combining datapaths: R-type and memory

Version 1: execute instruction in 1 clock cycle

No datapath resource can be used more than once in a single instruction

If needed more than once, must be duplicated

Separate instruction, data memory

Some resources can be shared between different instruction types

Need to have multiple inputs

Control signal to select which to use: multiplexor

Arithmetic-logical (R-type) and memory access (load/store) are similar in some ways

Differences

Second operand input to ALU:

Register contents for R-type

Sign-extended immediate value (offset) for load/store

Value stored in destination register:

ALU output for R-type

Data memory value for load

To combine datapaths:

Select source of second ALU operand

Select source of data to write to register

Use 2 MUXes with control inputs

ALUsrc for ALU

MemtoReg for register write

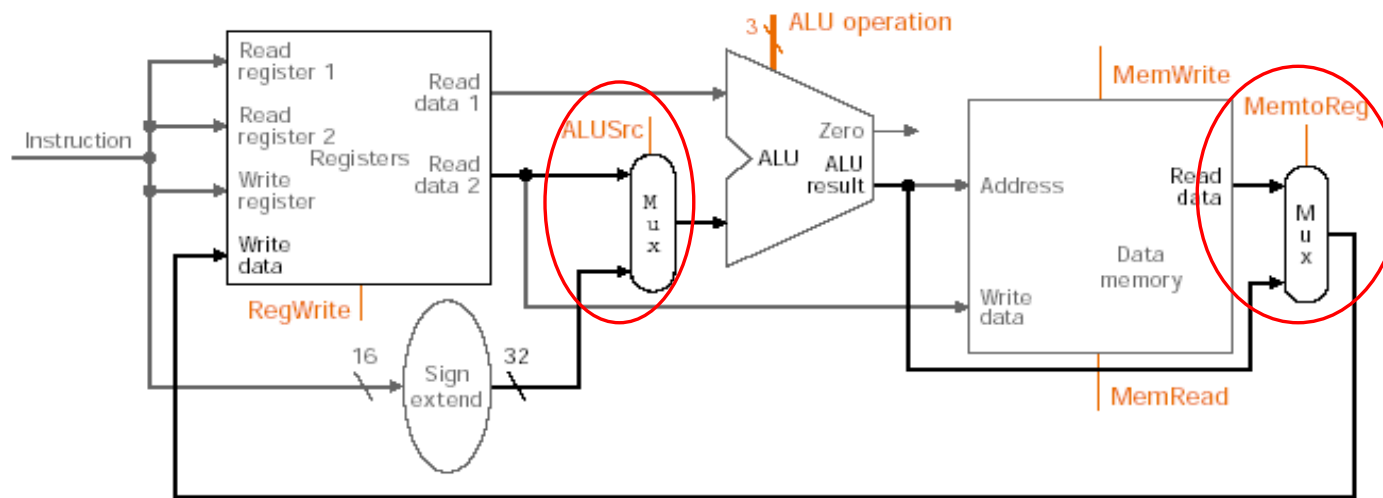


Fig. 5.11

Combining datapaths: instruction fetch

Can add instruction fetch:

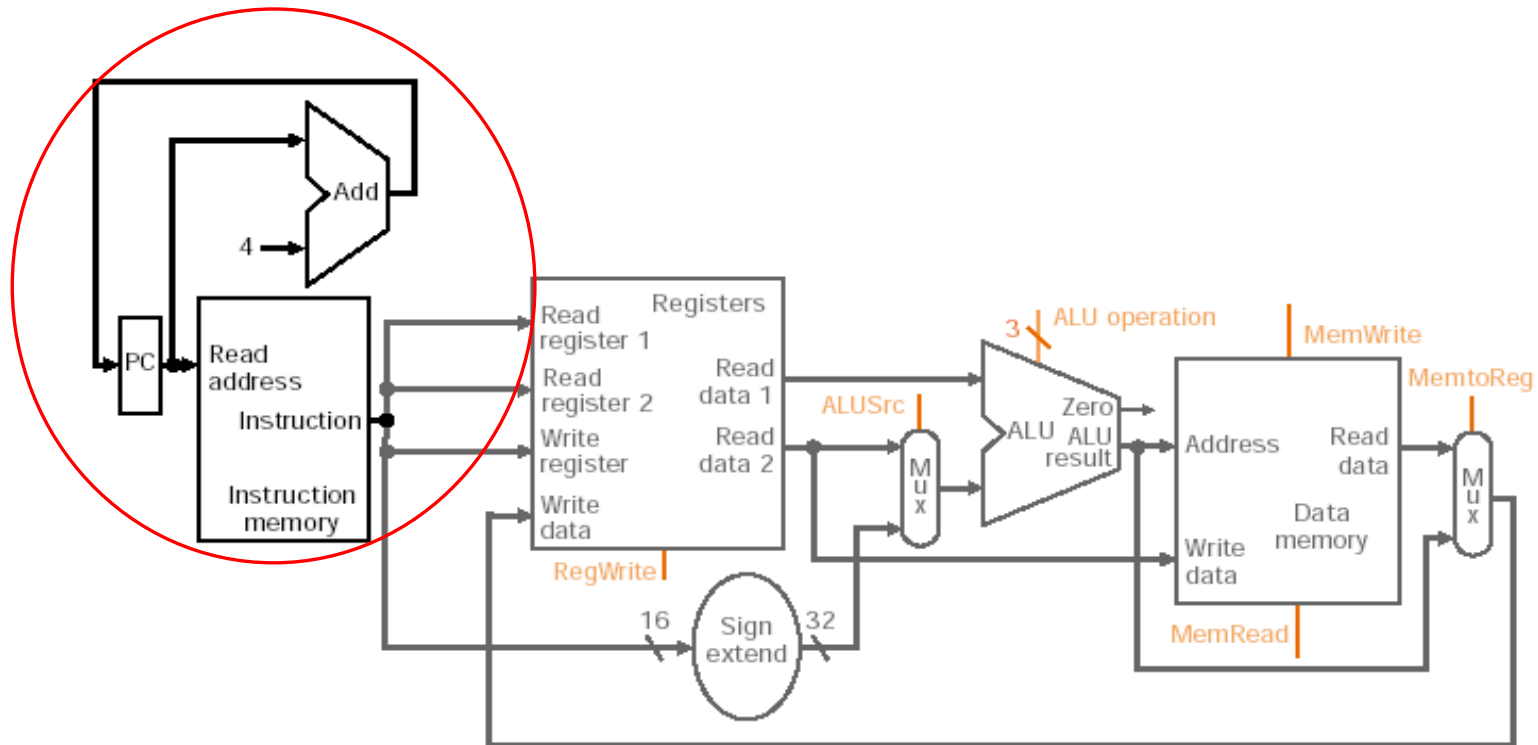


Fig. 5.12

Need separate adder in order to:
increment PC
perform ALU operation in same clock cycle

Combining datapaths: branch

Add branch:

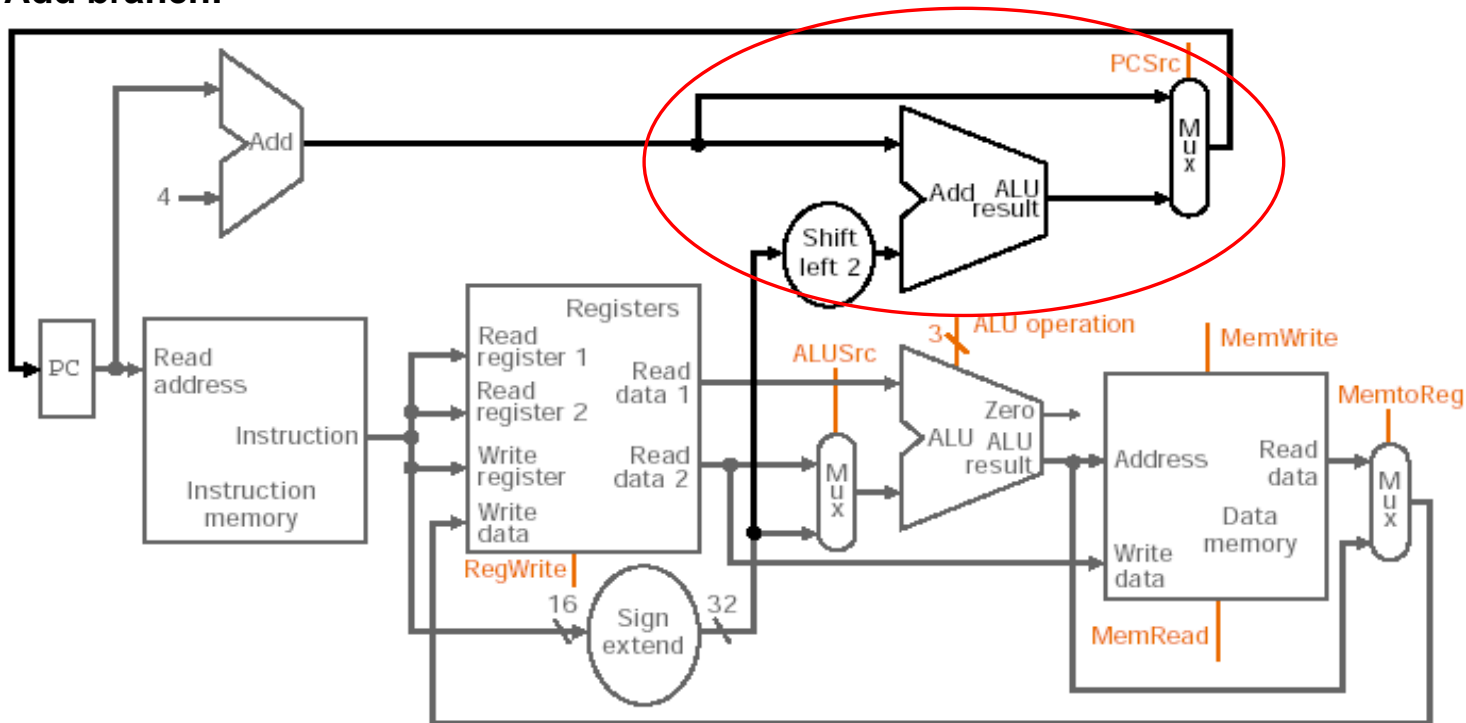


Fig. 5.13

Additional MUX

uses PCSrc input to select:

incremented PC or (PC + immediate) from second adder

output goes to update PC

Need to keep separate adder to compute branch address

Control unit

How to control the datapath?

Need to generate the control signals for MUXes, registers, and memory

Look at instruction formats

R-type	000000	\$rs	\$rt	\$rd	shamt	function
	b_{31-26}	b_{25-21}	b_{20-16}	b_{15-11}	b_{10-6}	b_{5-0}
memory	35 or 43	\$rs	\$rt	address		
	b_{31-26}	b_{25-21}	b_{20-16}	b_{15-0}		
branch	4	\$rs	\$rt	address		
	b_{31-26}	b_{25-21}	b_{20-16}	b_{15-0}		

Observations:

Opcode is always in upper 6 bits: Op[5-0], function in lower 6 bits: F[5-0]

Use to select operation to perform

Registers to read (\$rs, \$rt) always in bits 25-21 and 20-16

Use as indexes to register file for read

Base register for load/store always in bits 25-21

Offset always in bits 15-0


Destination register may be in 2 places:

bits 15-11 for R-type

bits 20-16 for load

Use as index to register file to write: need MUX to select

Control unit

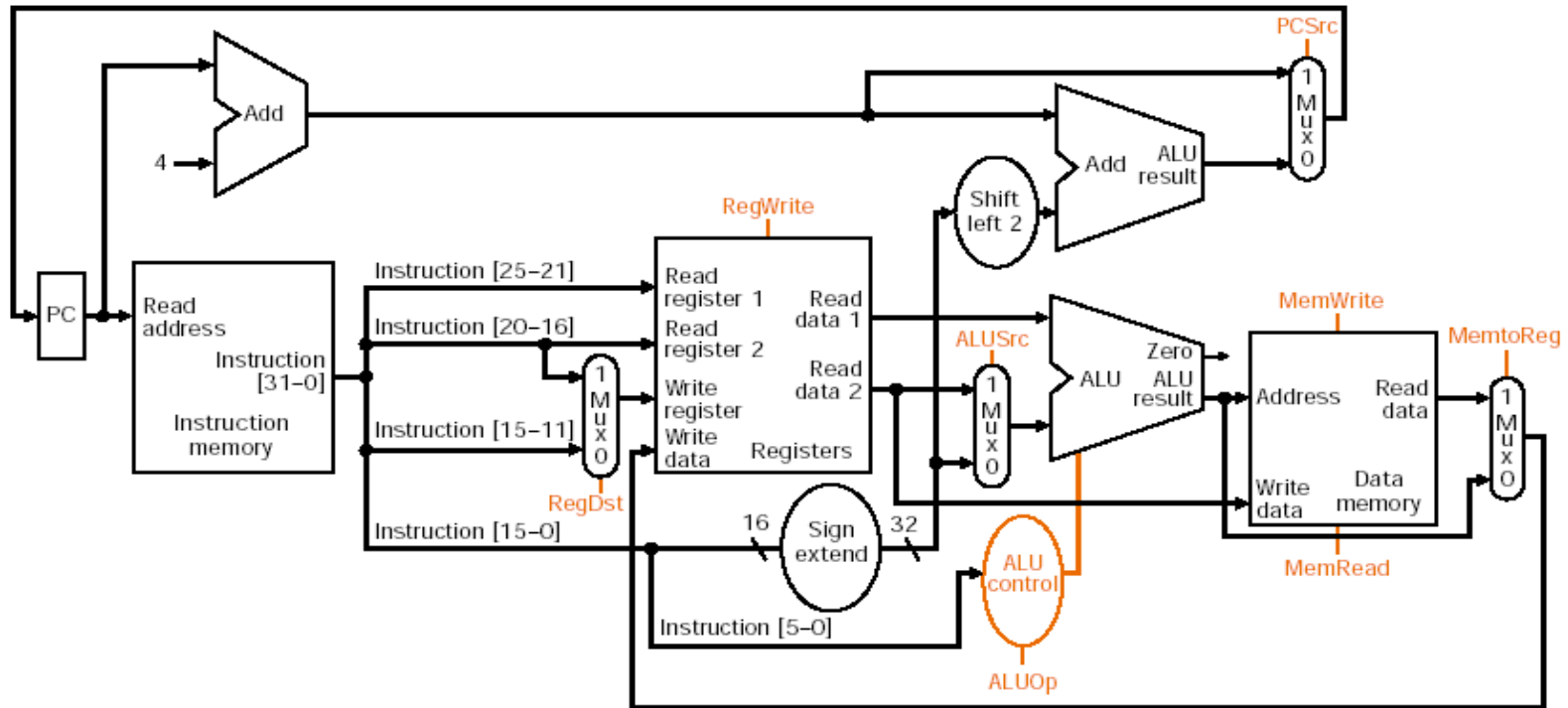

New features:

Instruction bit numbers for register numbers, opcode, function

MUX to select destination register

RegDst: selects \$rd or \$rt to write data

ALU control: uses function code and ALUOp to generate ALU operation selection


What is ALUOp? 2-bit code generated by main control (stay tuned)

Note that the values of RegDst, ALUSrc, and PCSrc are reversed in this diagram.

The version in the current printing of the text is correct.

Fig. 5.17

Control unit: main

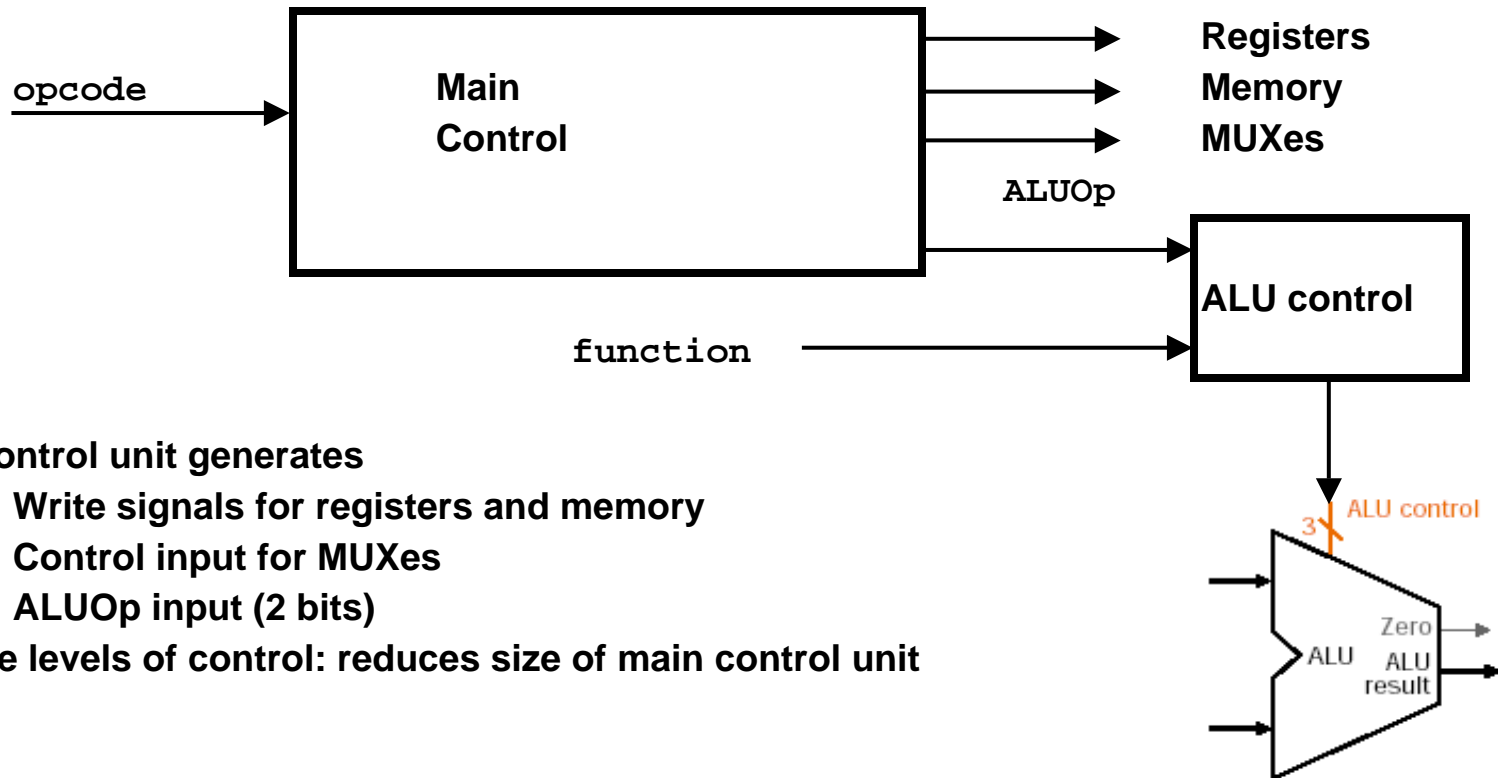

Main control unit generates

- Write signals for registers and memory

- Control input for MUXes

- ALUOp input (2 bits)

Multiple levels of control: reduces size of main control unit

Control unit: ALU

ALU operation selection: function depends on type of instruction

R-type: function determined by function field from instruction

Load/store: add to compute memory address

Branch: subtract to compare operands

Instruction	(Main control) ALUOp	(Instruction) Function	ALU control
lw, sw	00	xxxxxx	010 add
beq	01	xxxxxx	110 subtract
add	10	100000	010 add
sub	10	100010	110 subtract
and	10	100100	000 and
or	10	100101	001 or
slt	10	101010	111 set on less than

Fig. 5.15 shows complete truth table for generating these ALU control bits

Control unit: main

Main control signals

ALUOp: 2 bits based on op code used as input by ALU control

RegDst: selects from instruction bits 20-16 or 15-11 (\$rt or \$rd)
for destination register to write data

RegWrite: enables writing of destination register

ALUSrc: selects second input of ALU

0: Read data 2 from register file

1: sign-extended immediate from instruction

PCSrc: selects input to update PC

0: PC + 4 from adder

1: PC + offset from branch target calculation (other adder)

MemRead: data is read from data memory

MemWrite: data is written to data memory

MemtoReg: selects data to send to register file to write

0: ALU result


1: data read from memory

Can set all of these based only on opcode, except PCSrc

Should be set based on beq instruction AND ALU output is 0

Control unit generates Branch signal, which is ANDed with ALU Zero output

Datapath with control

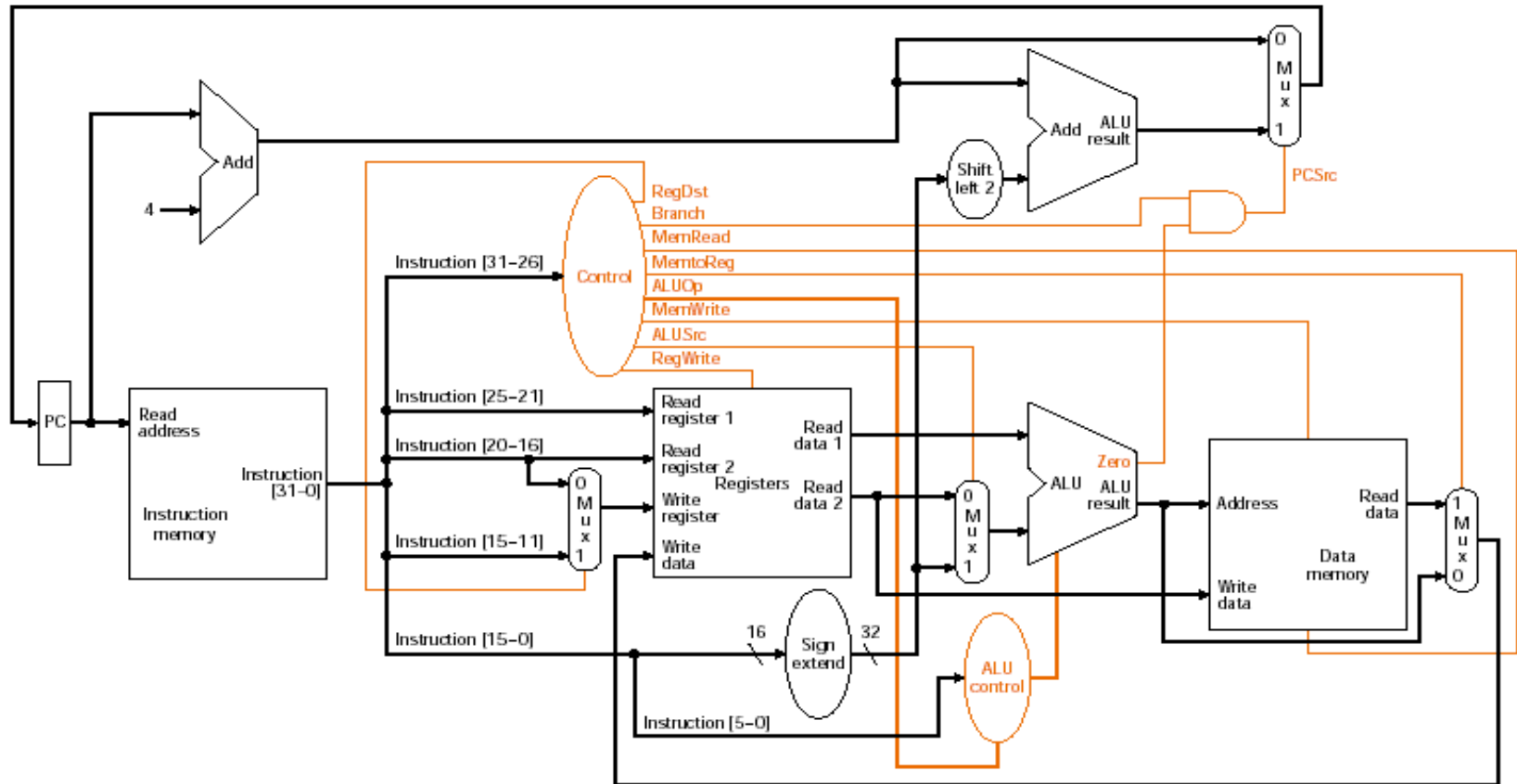

How to set control bits?

Could use Boolean equations or truth tables, but depends only on opcodes

Fig. 5.19

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

Fig. 5.20

Implementation in gates, using input from opcode bits, in Fig. C.5:

Opcode bits

Inputs




R-format lw sw beq

Outputs

RegDst
ALUSrc
MemtoReg
RegWrite
MemRead
MemWrite
Branch
ALUOp1
ALUOp0

Control signals

Datapath: R-type

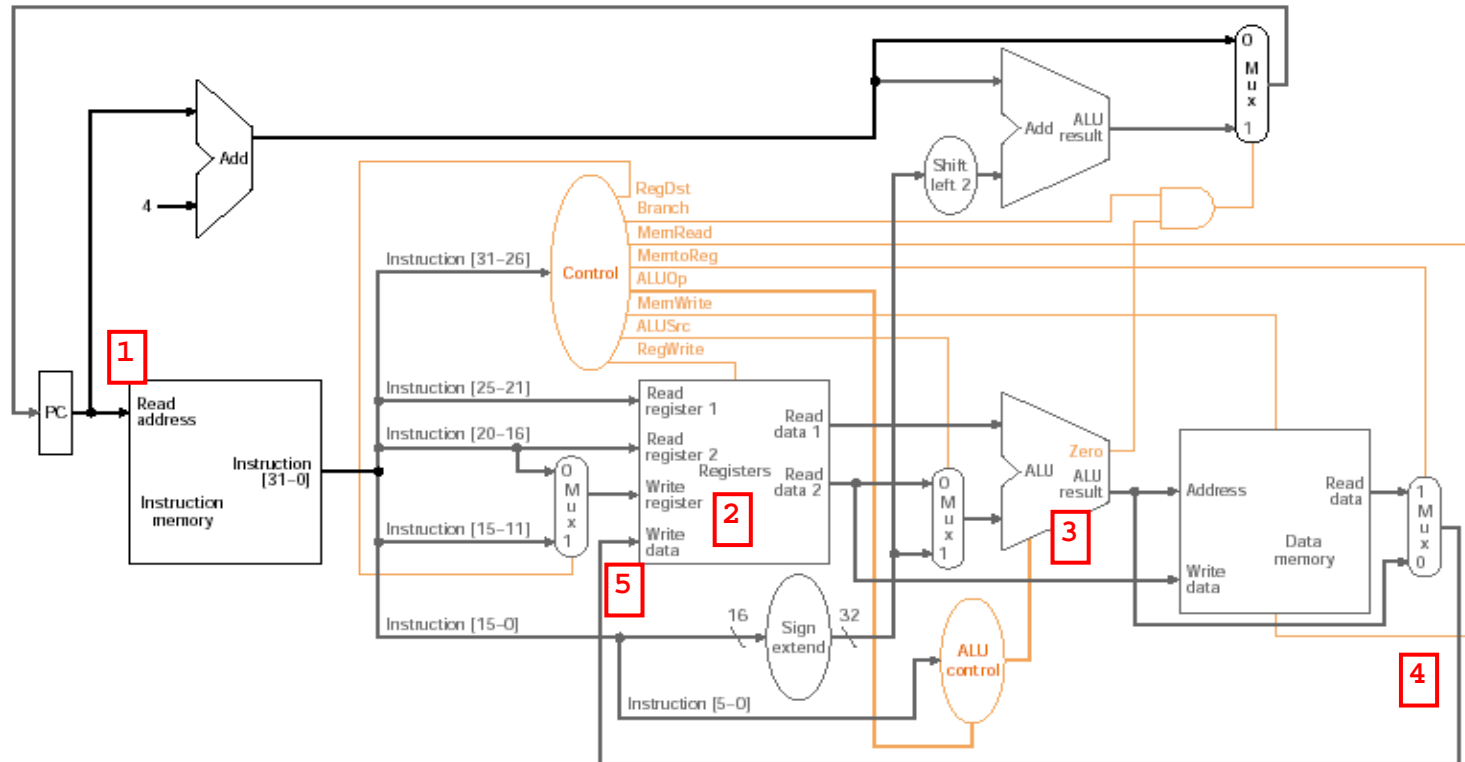

1. Fetch instruction and increment PC

2. Obtain operands from register file, based on source register numbers

3. Perform ALU operation, using ALU control to select, ALUSrc = 0

4. Select output from ALU using MemtoReg = 0

5. Write back to destination register (RegWrite = 1, RegDst = 1 for \$rd)

Note that this entire path is combinational, but the values are generated in the order shown.

Fig. 5.21

Datapath: memory access (load)

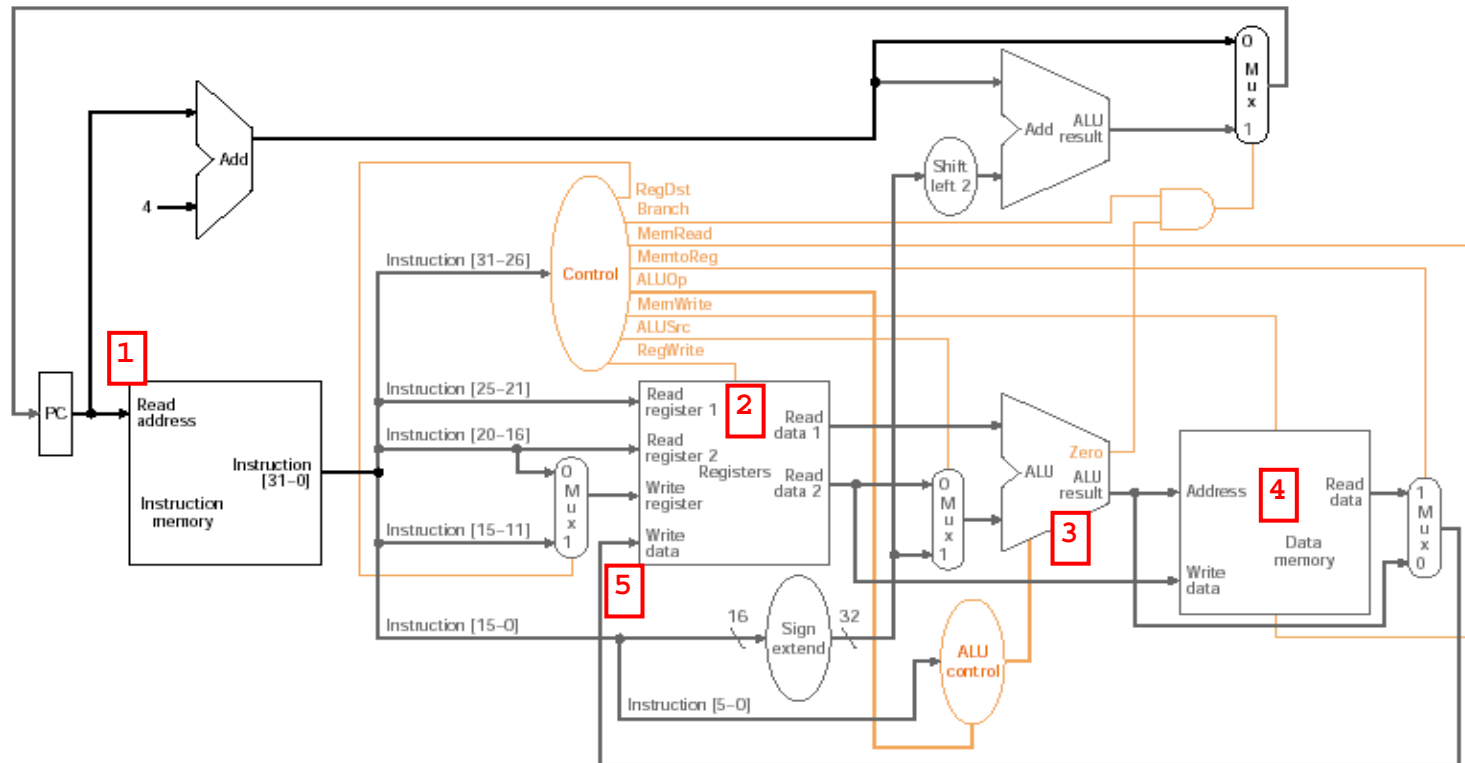



Fig. 5.21

1. Fetch instruction and increment PC
2. Obtain base register operand (Read data 1) from register file
3. Perform addition of register value with sign-extended immediate operand in ALU, using ALU control to select operation, ALUSrc = 1 to select immediate
4. Use ALU result as address for data memory
5. Use MemtoReg = 1 to select Read data and write back to destination register

Controls: RegWrite = 1, RegDst = 0 for \$rt

How would this have to change for a store instruction?

Datapath: memory access (store)

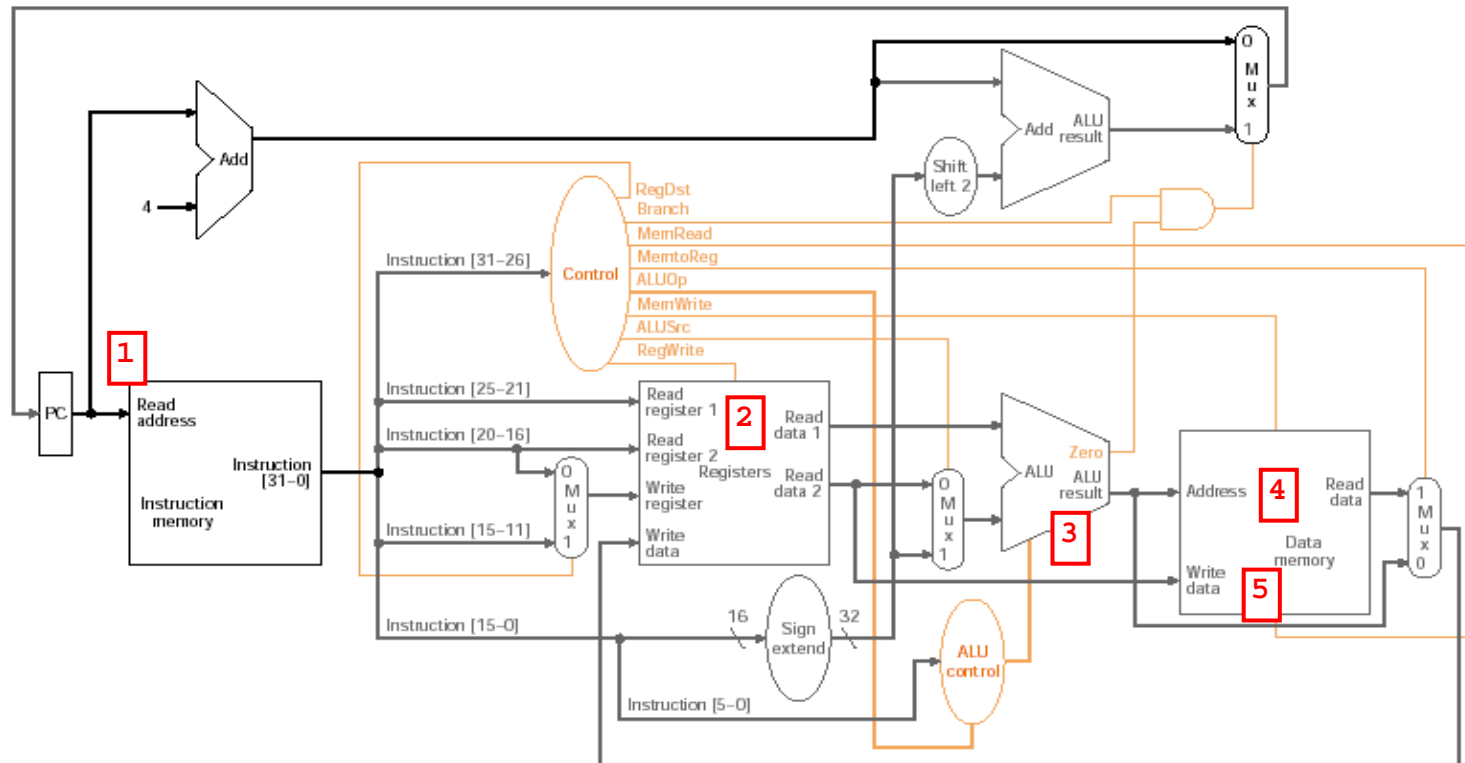

1. Fetch instruction and increment PC
2. Obtain base register (Read data 1) and data (Read data 2) from register file
3. Perform addition of register value with sign-extended immediate operand in ALU, using ALU control to select operation, ALUSrc = 1 to select immediate
4. Use ALU result as address for data memory
5. Using MemWrite = 1, write data operand to memory address

Note that MemtoReg and RegDst are don't cares

Fig. 5.21

Datapath: branch

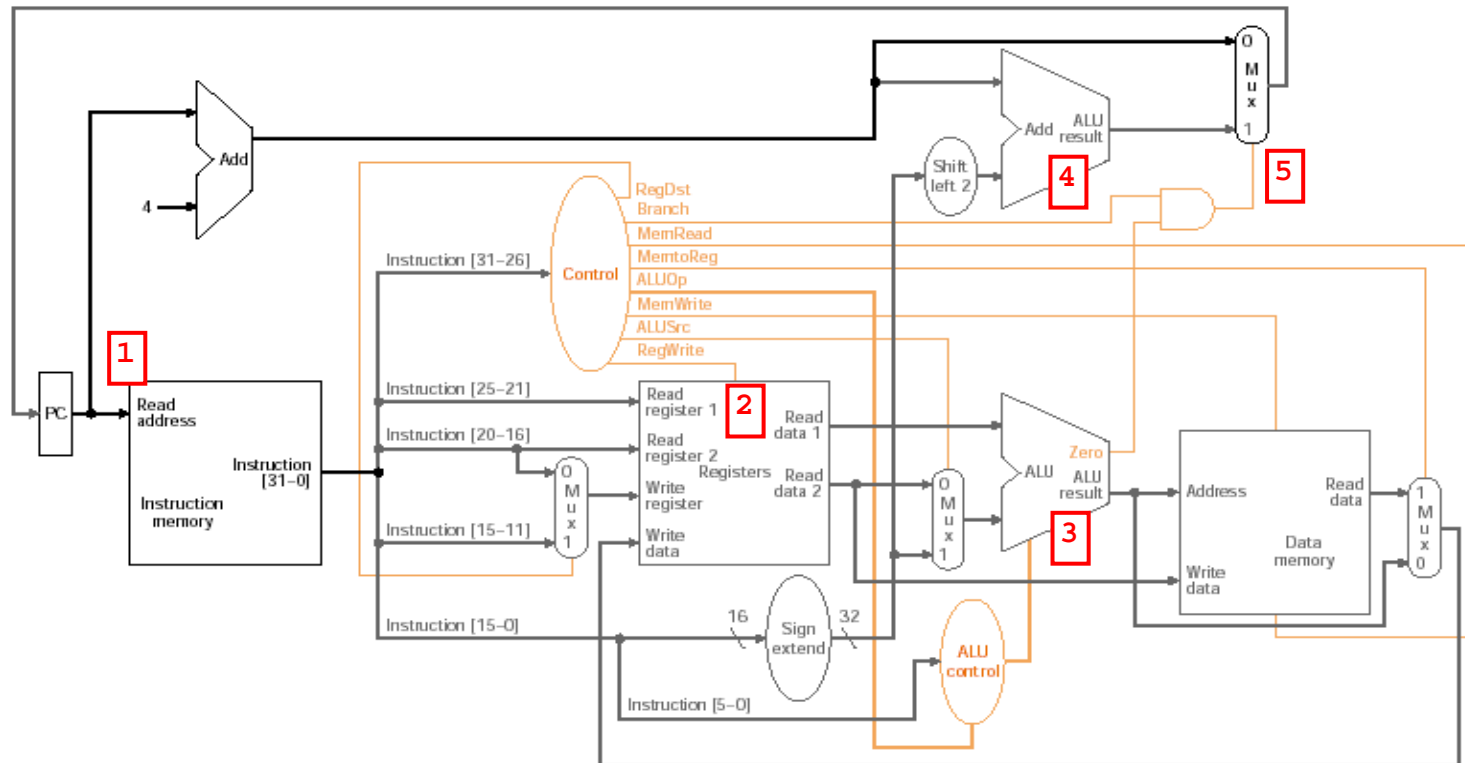


Fig. 5.21


1. Fetch instruction and increment PC
2. Read 2 registers from register file for comparison
3. ALU subtracts data values, using ALU control to select operation and ALUSrc = 0
4. Generate branch address: add (PC + 4) to sign-extended offset, shifted left by 2
why shifted by 2? what control signal values?
5. Use Zero output from ALU (and Branch control) to determine which result to use to update PC
If equal, use branch address
else use incremented PC

Note that this is all happening simultaneously in 1 clock cycle (adder separate from ALU)

Datapath: jump

Jump is still missing

Recall format:

 

Compare to branch:

computes target address differently

$PC \leftarrow PC_{31-28} :: IR_{25-0} :: 00$


update the PC by using:

- upper 4 bits of the program counter
- 26 bits of the target (lower 26 bits of instruction register)
- two 0's

(creates a 32-bit address)

unconditional

Datapath: jump

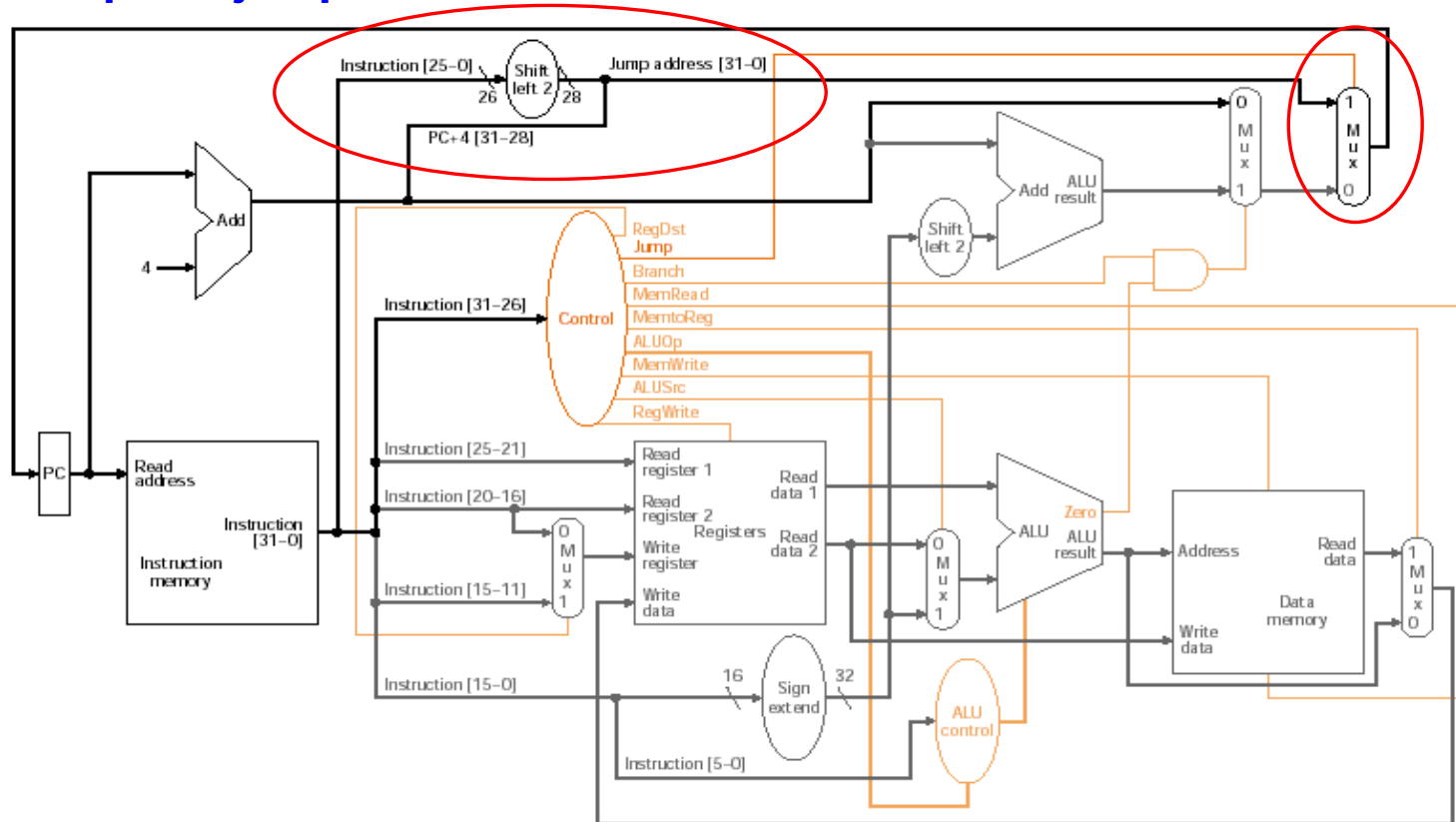


- Shift instruction bits 25-0 left 2 bits to create 28 bit value
- Combine with bits 31-28 of (PC + 4) to produce 32-bit jump address
- Additional MUX uses Jump control to select instruction address
- 0: Incremented PC or branch target
- 1: Jump address

Fig. 5.29

Datapath: critical path

Why don't we use single-cycle datapath? Too slow!

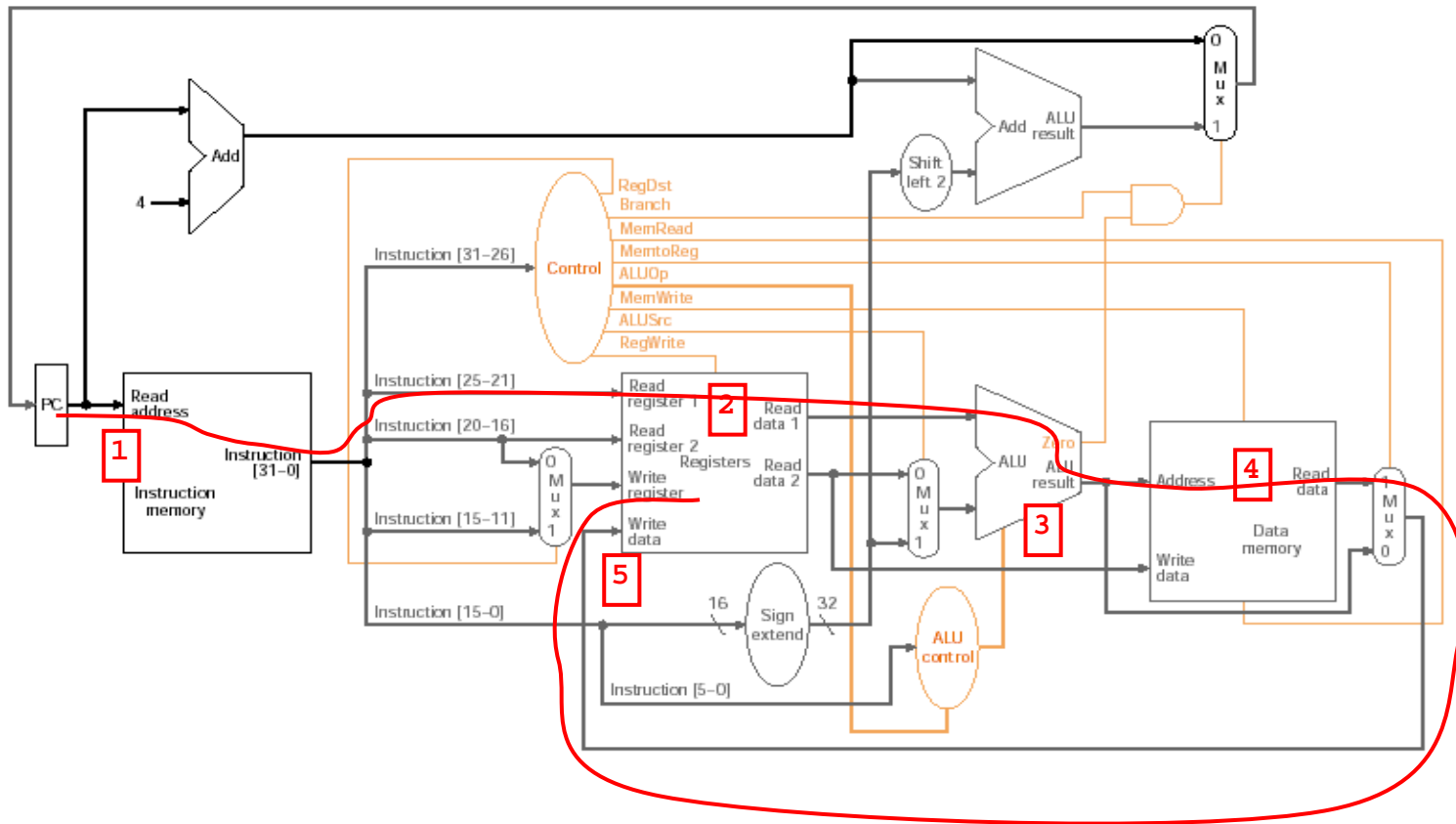Clock cycle time must be as long as the longest path: load instruction



5 functional units: PC, instruction memory, register file, ALU, data memory, plus 2 MUXes

Datapath: performance

Single-cycle performance

Suppose operation times are:

Memory: 2 nanoseconds

ALU/adders: 2 ns

Register file (read or write): 1 ns

Assume MUXes, control units, PC access, sign-extend have no delay

How long must the clock cycle be?

Instruction type	Inst mem	Reg read	ALU op	Data mem	Reg write	Total	Distribution
R-type	2	1	2	0	1	6	44%
load	2	1	2	2	1	8	24%
store	2	1	2	2	0	7	12%
branch	2	1	2	0	0	5	18%
jump	2	0	0	0	0	2	2%

With single-cycle, clock period must be 8 ns

But, not all instructions are loads! Suppose distribution of instruction types shown.

If we could vary the instruction time, the average would be:

$$(6 * 44\%) + (8 * 24\%) + (7 * 12\%) + (5 * 18\%) + (2 * 2\%) = 6.3$$

This is 27% faster!

Datapath: performance

Average instruction time could be less if we didn't have to use load instruction to determine cycle time

But that's not actually the longest instruction time!

What about multiply and divide, or even floating-point operations?

Need separate, slower ALUs

Assume: 8 ns for floating-point add, 16 ns for floating-point multiply

Instruction type	Inst mem	Reg read	ALU op	Data mem	Reg write	Total	Distribution
R-type	2	1	2	0	1	6	27%
load	2	1	2	2	1	8	31%
store	2	1	2	2	0	7	21%
branch	2	1	2	0	0	5	5%
jump	2	0	0	0	0	2	2%
FP add	2	1	8	0	1	12	7%
FP multiply	2	1	16	0	1	20	7%

Average is 8.1 ns, which is only $8.1/20 = 41\%$ of the single-cycle time
In other words, variable cycle could be about 2.5 times faster!

Variable clock cycle is impractical, but we can break up the instructions into shorter cycles, then only use the parts needed for any given instruction

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.