

CS:APP Chapter 4 Computer Architecture Logic Design


Randal E. Bryant

Carnegie Mellon University

<http://csapp.cs.cmu.edu>

CS:APP

Digital Signals

 

- Use voltage thresholds to extract discrete values from continuous signal
- Simplest version: 1-bit signal
 - Either high range (1) or low range (0)
 - With guard range between them
- Not strongly affected by noise or low quality circuit elements
 - Can make circuits simple, small, and fast

- 3 -

CS:APP

Overview of Logic Design

Fundamental Hardware Requirements

- Communication
 - How to get values from one place to another
- Computation
- Storage


Bits are Our Friends

- Everything expressed in terms of values 0 and 1
- Communication
 - Low or high voltage on wire
- Computation
 - Compute Boolean functions
- Storage
 - Store bits of information


- 2 -

CS:APP

Computing with Logic Gates

 

 
- Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs
 - With some, small delay



- 4 -

CS:APP


Combinational Circuits

 

Acyclic Network of Logic Gates

- Continuously responds to changes on primary inputs
- Primary outputs become (after some delay) Boolean functions of primary inputs

Bit Equality

 

HCL Expression


```
bool eq = (a&&b) || (!a&&!b)
```

- Generate 1 if a and b are equal

Hardware Control Language (HCL)

- Very simple hardware description language
 - Boolean operations have syntax similar to C logical operations
- We'll use it to describe control logic for processors

Word Equality

 


HCL Representation

```
bool Eq = (A == B)
```

- 32-bit word size
- HCL representation
 - Equality operation
 - Generates Boolean value

Bit-Level Multiplexor

 


HCL Expression


```
bool out = (s&&a) || (!s&&b)
```

- Control signal s
- Data signals a and b
- Output a when s=1, b when s=0

Word Multiplexor

 

Word-Level Representation

 


HCL Representation

```
int Out = [
  s : A;
  !s : B;
];
```

- Select input word A or B depending on control signal s
- HCL representation
 - Case expression
 - Series of test : value pairs
 - Output value for first successful test

HCL Word-Level Examples


Minimum of 3 Words

 

```
int Min3 = [
  A < B && A < C : A;
  B < A && B < C : B;
  1 : C;
];
```

- Find minimum of three input words
- HCL case expression
- Final case guarantees match


4-Way Multiplexor

 

```
int Out4 = [
  !s1&&!s0: D0;
  !s1      : D1;
  !s0      : D2;
  1        : D3;
];
```

- Select one of 4 inputs based on two control bits
- HCL case expression
- Simplify tests by assuming sequential matching




Arithmetic Logic Unit

 

- Combinational logic
 - Continuously responding to inputs
- Control signal selects function computed
 - Corresponding to 4 arithmetic/logical operations in Y86
- Also computes values for condition codes



Storing 1 Bit

Bistable Element

   


Storing 1 Bit (cont.)

Bistable Element

  


Physical Analogy

 


Storing and Accessing 1 Bit


Bistable Element

 


R-S Latch

 


Resetting

 

Setting

 


Storing

 


1-Bit Latch


D Latch

 

Latching

 


Storing

 


Transparent 1-Bit Latch

Latching


 


Changing D

 



- When in latching mode, combinational propagation from D to Q+ and Q-
- Value latched depends on value of D as C falls

Edge-Triggered Latch

  

- Only in latching mode for brief period
 - Rising clock edge
- Value latched depends on data as clock rises
- Output remains stable at all other times

Registers

  


- Stores word of data
 - Different from *program registers* seen in assembly code
- Collection of edge-triggered latches
- Loads input on rising edge of clock

Register Operation




- Stores data bits
- For most of time acts as barrier between input and output
- As clock rises, loads input

State Machine Example

 

 
- Accumulator circuit
- Load or accumulate on each cycle



- 21 -

CS:APP

Random-Access Memory

 


- Stores multiple words of memory
 - Address input specifies which word to read or write
- Register file
 - Holds values of program registers
 - `%eax`, `%esp`, etc.
 - Register identifier serves as address
 - » ID 8 implies no read or write performed
- Multiple Ports
 - Can read and/or write multiple words in one cycle
 - » Each has separate address and data input/output

- 22 -

CS:APP

Register File Timing

 


Reading

- Like combinational logic
- Output data generated based on input address
 - After some delay

Writing

 - Like register
- Update only as clock rises



- 23 -

CS:APP

Hardware Control Language

- Very simple hardware description language
- Can only express limited aspects of hardware operation
 - Parts we want to explore and modify

Data Types

- `bool`: Boolean
 - `a`, `b`, `c`, ...
- `int`: words
 - `A`, `B`, `C`, ...
 - Does not specify word size---bytes, 32-bit words, ...

Statements

- `bool a = bool-expr ;`
- `int A = int-expr ;`

- 24 -

CS:APP

HCL Operations

- Classify by type of value returned

Boolean Expressions

- Logic Operations
 - `a && b, a || b, !a`
- Word Comparisons
 - `A == B, A != B, A < B, A <= B, A >= B, A > B`
- Set Membership
 - `A in { B, C, D }`
 - » Same as `A == B || A == C || A == D`

Word Expressions

- Case expressions
 - `[a : A; b : B; c : C]`
 - Evaluate test expressions `a, b, c, ...` in sequence
 - Return word expression `A, B, C, ...` for first successful test

Summary

Computation

- Performed by combinational logic
- Computes Boolean functions
- Continuously reacts to input changes

Storage

- Registers
 - Hold single words
 - Loaded as clock rises
- Random-access memories
 - Hold multiple words
 - Possible multiple read or write ports
 - Read word when address input changes
 - Write word as clock rises